

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$a' \cdot b \cdot c \cdot d'$$

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$a' \cdot b \cdot c \cdot d'$$

$$a \cdot b' \cdot c' \cdot d'$$

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$a' \cdot b \cdot c \cdot d'$$

$$a \cdot b' \cdot c' \cdot d'$$

$$a \cdot b' \cdot c' \cdot d$$

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$a' \cdot b \cdot c \cdot d'$$

$$a \cdot b' \cdot c' \cdot d'$$

$$a \cdot b' \cdot c' \cdot d$$

$$a \cdot b' \cdot c \cdot d'$$

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$a' \cdot b \cdot c \cdot d'$$

$$a \cdot b' \cdot c' \cdot d'$$

$$a \cdot b' \cdot c' \cdot d$$

$$a \cdot b' \cdot c \cdot d'$$

$$a \cdot b' \cdot c \cdot d$$

$$a \cdot b \cdot c' \cdot d'$$

$$a \cdot b \cdot c' \cdot d$$

$$a \cdot b \cdot c \cdot d'$$

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$a' \cdot b \cdot c \cdot d'$$

$$a \cdot b' \cdot c' \cdot d'$$

$$a \cdot b' \cdot c' \cdot d$$

$$a \cdot b' \cdot c \cdot d'$$

$$a \cdot b' \cdot c \cdot d$$

$$a \cdot b \cdot c' \cdot d'$$

$$a \cdot b \cdot c' \cdot d$$

$$a \cdot b \cdot c \cdot d'$$

} or

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

		ab			
		00	01	11	10
cd	00				
	01				
	11				
	10				

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

		ab			
		00	01	11	10
cd	00	0			
	01				
	11				
	10				

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

		ab			
		00	01	11	10
cd	00	0			1
	01				
	11				
	10				

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

		ab			
		00	01	11	10
cd	00	0			1
	01				
	11			0	
	10				

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

		ab			
		00	01	11	10
cd	00	0			1
	01				
	11			0	
	10		1		

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

		ab			
		00	01	11	10
cd	00	0	0	1	1
	01	0	0	1	1
	11	0	0	0	1
	10	0	1	1	1

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

		ab			
		00	01	11	10
cd	00	0	0	1	1
	01	0	0	1	1
	11	0	0	0	1
	10	0	1	1	1

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

		ab				cd	$a \cdot b'$
		00	01	11	10		
cd	00	0	0	1	1		
	01	0	0	1	1		
	11	0	0	0	1		
	10	0	1	1	1		

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

		ab			
		00	01	11	10
cd	00	0	0	1	1
	01	0	0	1	1
	11	0	0	0	1
	10	0	1	1	1

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

		ab			
		00	01	11	10
cd	00	0	0	1	1
	01	0	0	1	1
	11	0	0	0	1
	10	0	1	1	1
		$b \cdot c \cdot d'$			

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

		ab			
		00	01	11	10
cd	00	0	0	1	1
	01	0	0	1	1
	11	0	0	0	1
	10	0	1	1	1

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

		ab				
		00	01	11	10	
cd	00	0	0	1	1	$a \cdot c'$
	01	0	0	1	1	
	11	0	0	0	1	
	10	0	1	1	1	

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

		ab			
		00	01	11	10
cd	00	0	0	1	1
	01	0	0	1	1
	11	0	0	0	1
	10	0	1	1	1

$$e = a \cdot b' + b \cdot c \cdot d' + a \cdot c'$$

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$a' \cdot b \cdot c \cdot d'$$

$$a \cdot b' \cdot c' \cdot d'$$

$$a \cdot b' \cdot c' \cdot d$$

$$a \cdot b' \cdot c \cdot d'$$

$$a \cdot b' \cdot c \cdot d$$

$$a \cdot b \cdot c' \cdot d'$$


$$a \cdot b \cdot c' \cdot d$$

$$a \cdot b \cdot c \cdot d'$$


Circuits

A **circuit** is a collection of logical gates that transforms a set of binary inputs into a set of binary outputs.

Circuits

 


Circuits

 


$$c = (a + b)$$

Circuits

 

Circuits

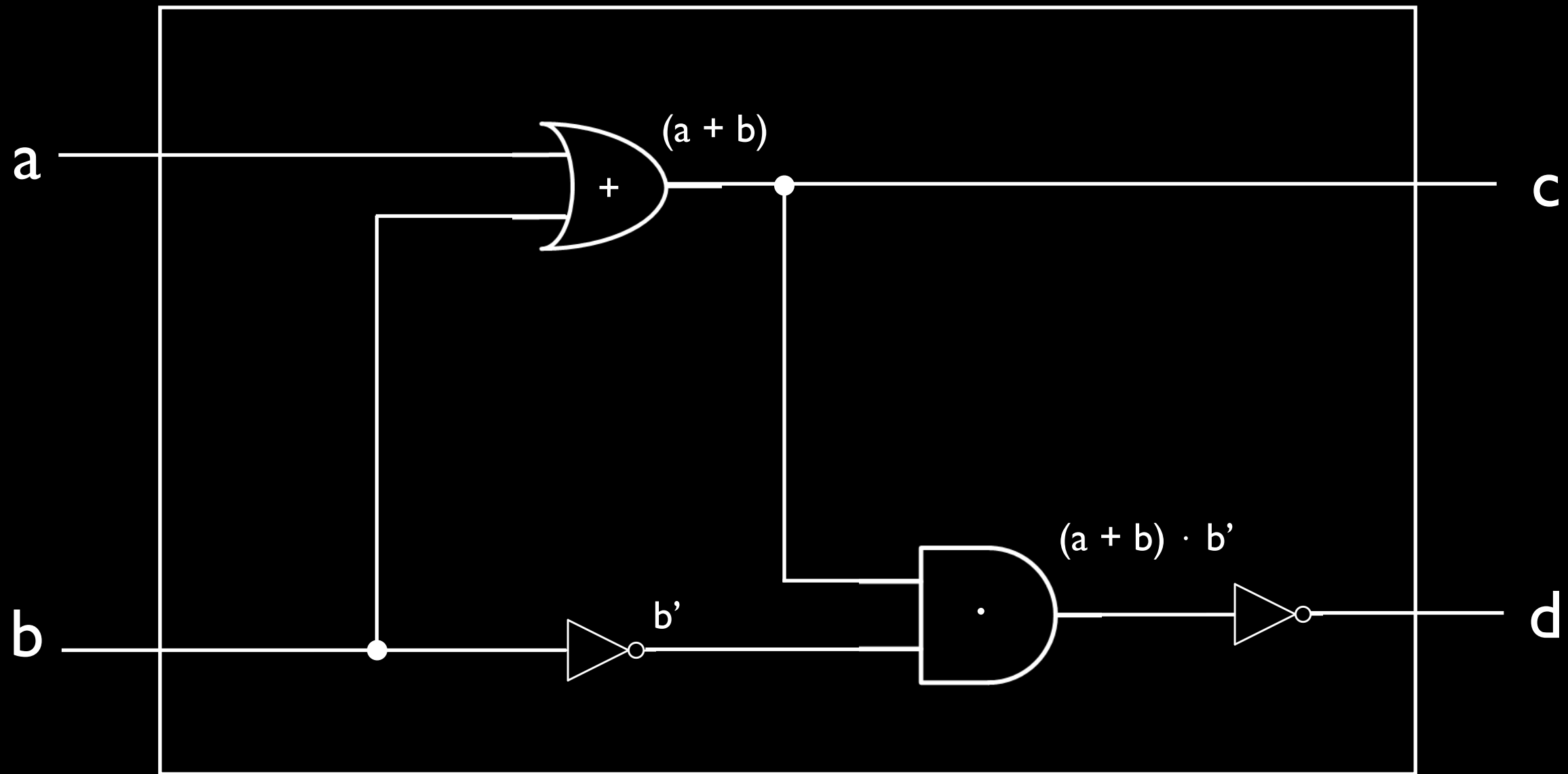

$$d = ((a + b) \cdot b')'$$

Designing Circuits

input		output	
a	b	c	d
0	0		
0	1		
1	0		
1	1		

step 1. build truth-table for all possible input/output values

Designing Circuits

input		output	
a	b	c	d
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

arbitrary, for now

step 1. build truth-table for all possible input/output values

Designing Circuits

input		output	
a	b	c	d
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

arbitrary, for now

step 2. build sub-expressions with *and/not* for each output column

Designing Circuits

input		output	
a	b	c	d
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$d = a \cdot b$$

step 2. build sub-expressions with *and/not* for each output column

Designing Circuits

input		output	
a	b	c	d
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$c = a' \cdot b$$

step 2. build sub-expressions with *and/not* for each output column

Designing Circuits

input		output	
a	b	c	d
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$c = a' \cdot b$$

$$c = a \cdot b'$$

step 2. build sub-expressions with *and/not* for each output column

Designing Circuits

input		output	
a	b	c	d
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

step 3. combine, two at a time, sub-expressions with an *or*

Designing Circuits

input		output	
a	b	c	d
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$c = (a' \cdot b) + (a \cdot b')$$

step 3. combine, two at a time, sub-expressions with an *or*

Designing Circuits


input		output	
a	b	c	d
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$c = (a' \cdot b) + (a \cdot b')$$

$$d = a \cdot b$$


step 3. combine, two at a time, sub-expressions with an *or*

Designing Circuits

 


step 4. draw circuit diagram

Designing Circuits

 

step 4. draw circuit diagram

Designing Circuits

 

step 4. draw circuit diagram

Designing Circuits

- step 1. build truth-table for all possible input/output values
- step 2. build sub-expressions with *and/not* for each output column
- step 3. combine, two at a time, sub-expressions with an *or*
- step 4. draw circuit diagram

1-Bit Compare for Equality (CE)

```
if two bits  $a, b$  are equal then  
    return 1  
else  
    return 0
```

1-Bit Compare for Equality (CE)

input		output
a	b	c
0	0	
0	1	
1	0	
1	1	

1-Bit Compare for Equality (CE)

input		output
a	b	c
0	0	1
0	1	0
1	0	0
1	1	1

1-Bit Compare for Equality (CE)

input		output	
a	b	c	sub-expression
0	0	1	
0	1	0	
1	0	0	
1	1	1	

1-Bit Compare for Equality (CE)

input		output	
a	b	c	sub-expression
0	0	1	$a' \cdot b'$
0	1	0	
1	0	0	
1	1	1	$a \cdot b$

1-Bit Compare for Equality (CE)

input		output	
a	b	c	sub-expression
0	0	1	$a' \cdot b'$
0	1	0	
1	0	0	
1	1	1	$a \cdot b$

$$c = (a' \cdot b') + (a \cdot b)$$

1-Bit Compare for Equality (CE)

input

a


b

output

c


$$c = (a' \cdot b') + (a \cdot b)$$

1-Bit Compare for Equality (CE)

 


$$c = (a' \cdot b') + (a \cdot b)$$

1-Bit Compare for Equality (CE)

 

$$c = (a' \cdot b') + (a \cdot b)$$

1-Bit Compare for Equality (CE)

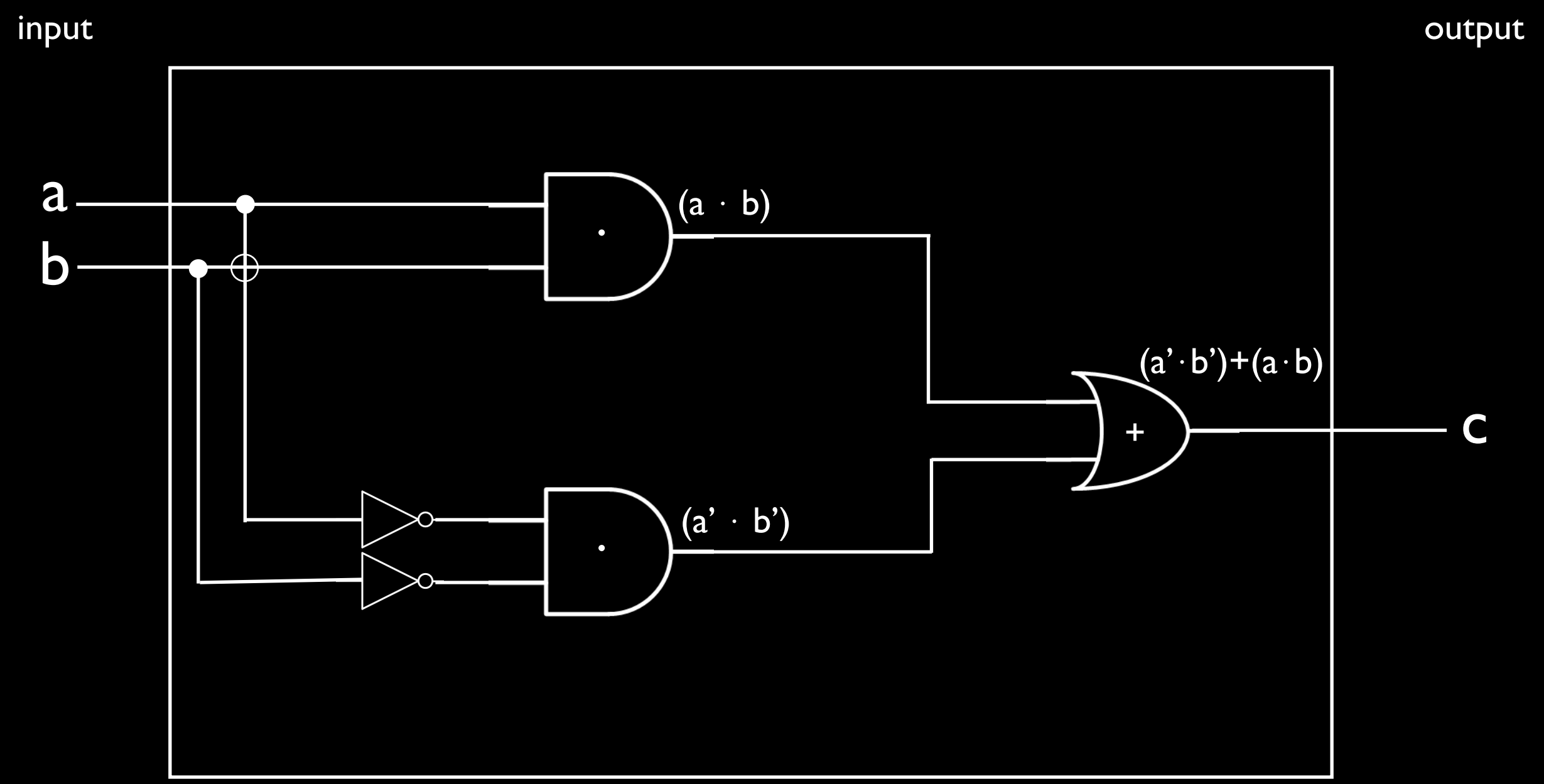

$$c = (a' \cdot b') + (a \cdot b)$$

4-Bit Compare for Equality (CE)

```
If two 4-bit numbers are equal then  
    return 1  
else  
    return 0
```

4-Bit Compare for Equality (CE)

```
If two 4-bit numbers are equal then  
    return 1  
else  
    return 0
```


$$a_3 a_2 a_1 a_0 == b_3 b_2 b_1 b_0$$

4-Bit Compare for Equality (CE)

input				output				
a ₃	a ₂	a ₁	a ₀	b ₃	b ₂	b ₁	b ₀	c

how many rows?

4-Bit Compare for Equality (CE)

 

256

4-Bit Compare for Equality (CE)

two 4-bit numbers are equal if:

$a_3 == b_3$ and


$a_2 == b_2$ and

$a_1 == b_1$ and



$a_0 == b_0$

$$a_3\ a_2\ a_1\ a_0 == b_3\ b_2\ b_1\ b_0$$

4-Bit Compare for Equality (CE)

 

4-Bit Compare for Equality (CE)

  

4-Bit Compare for Equality (CE)

input

output

a₃

b₃

a₂

b₂

a₁


b₁

a₀

b₀

c


4-Bit Compare for Equality (CE)

 


4-Bit Compare for Equality (CE)




4-Bit Compare for Equality (CE)

 

4-Bit Compare for Equality (CE)

 

4-Bit Compare for Equality (CE)

 

1-Bit Adder

build a circuit that adds two 1-bit numbers

1-Bit Adder

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = ?$$

1-Bit Adder

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10 \quad \textit{need to carry}$$

1-Bit Adder

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10$$

input: two digits a, b

1-Bit Adder

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10$$

input: two digits a, b and a carry c

1-Bit Adder

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10$$

output: sum d and carry e

1 -Bit Adder

$$\begin{array}{r} 5 \\ 1 \\ \hline 6 \end{array}$$

$$\begin{array}{r} 101 \\ 001 \\ \hline \end{array}$$

$$\begin{array}{r} 2^2 + 2^0 \\ 2^0 \end{array}$$

1 -Bit Adder

$$\begin{array}{r} 5 \\ 1 \\ \hline 6 \end{array}$$

$$\begin{array}{r} 1 \\ 101 \\ 001 \\ \hline 0 \end{array}$$

1 -Bit Adder

$$\begin{array}{r} 5 \\ 1 \\ \hline 6 \end{array}$$

$$\begin{array}{r} 1 \\ 101 \\ 001 \\ \hline 10 \end{array}$$

1 -Bit Adder

	1	
5	101	
1	001	
---	---	
6	110	

1-Bit Adder

	1	
5	101	
1	001	
---	---	
6	110	$2^2 + 2^1$

1-Bit Adder

input: digits a , b and carry c

output: sum d and carry e

1-Bit Adder

a	b	c	d	e
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

input: digits a , b and carry c

output: sum d and carry e

1-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

input: digits a , b and carry c

output: sum d and carry e

1-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1	1	0
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

input: digits a , b and carry c

output: sum d and carry e

1-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

input: digits a , b and carry c

output: sum d and carry e

1-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0		
1	0	1		
1	1	0		
1	1	1		

input: digits a , b and carry c

output: sum d and carry e

1-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1		
1	1	0		
1	1	1		

input: digits a , b and carry c

output: sum d and carry e

1-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0		
1	1	1		

input: digits a , b and carry c

output: sum d and carry e

1-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1		

input: digits a , b and carry c

output: sum d and carry e

1-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

input: digits a , b and carry c

output: sum d and carry e

1-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0		
0	1	0	1	0		
0	1	1	0	1		
1	0	0	1	0		
1	0	1	0	1		
1	1	0	0	1		
1	1	1	1	1		

1-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0		
0	1	0	1	0		
0	1	1	0	1		
1	0	0	1	0		
1	0	1	0	1		
1	1	0	0	1		
1	1	1	1	1		

1-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0	$a' \cdot b' \cdot c$	
0	1	0	1	0		
0	1	1	0	1		
1	0	0	1	0		
1	0	1	0	1		
1	1	0	0	1		
1	1	1	1	1		

1-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0	$a' \cdot b' \cdot c$	
0	1	0	1	0	$a' \cdot b \cdot c'$	
0	1	1	0	1		
1	0	0	1	0		
1	0	1	0	1		
1	1	0	0	1		
1	1	1	1	1		

1-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0	$a' \cdot b' \cdot c$	
0	1	0	1	0	$a' \cdot b \cdot c'$	
0	1	1	0	1		
1	0	0	1	0	$a \cdot b' \cdot c'$	
1	0	1	0	1		
1	1	0	0	1		
1	1	1	1	1		

1-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0	$a' \cdot b' \cdot c$	
0	1	0	1	0	$a' \cdot b \cdot c'$	
0	1	1	0	1		
1	0	0	1	0	$a \cdot b' \cdot c'$	
1	0	1	0	1		
1	1	0	0	1		
1	1	1	1	1	$a \cdot b \cdot c$	

1-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0	$a' \cdot b' \cdot c$	
0	1	0	1	0	$a' \cdot b \cdot c'$	
0	1	1	0	1		$a' \cdot b \cdot c$
1	0	0	1	0	$a \cdot b' \cdot c'$	
1	0	1	0	1		$a \cdot b' \cdot c$
1	1	0	0	1		$a \cdot b \cdot c'$
1	1	1	1	1	$a \cdot b \cdot c$	$a \cdot b \cdot c$

1-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0	$a' \cdot b' \cdot c$	
0	1	0	1	0	$a' \cdot b \cdot c'$	
0	1	1	0	1		$a' \cdot b \cdot c$
1	0	0	1	0	$a \cdot b' \cdot c'$	
1	0	1	0	1		$a \cdot b' \cdot c$
1	1	0	0	1		$a \cdot b \cdot c'$
1	1	1	1	1	$a \cdot b \cdot c$	$a \cdot b \cdot c$


$$d = (a' \cdot b' \cdot c) + (a' \cdot b \cdot c') + (a \cdot b' \cdot c') + (a \cdot b \cdot c)$$

1-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0	$a' \cdot b' \cdot c$	
0	1	0	1	0	$a' \cdot b \cdot c'$	
0	1	1	0	1		$a' \cdot b \cdot c$
1	0	0	1	0	$a \cdot b' \cdot c'$	
1	0	1	0	1		$a \cdot b' \cdot c$
1	1	0	0	1		$a \cdot b \cdot c'$
1	1	1	1	1	$a \cdot b \cdot c$	$a \cdot b \cdot c$

$$e = (a' \cdot b \cdot c) + (a \cdot b' \cdot c) + (a \cdot b \cdot c') + (a \cdot b \cdot c)$$

1-Bit Adder

 


a b c


4-Bit Adder

build a circuit that adds two 4-bit numbers


4-Bit Adder

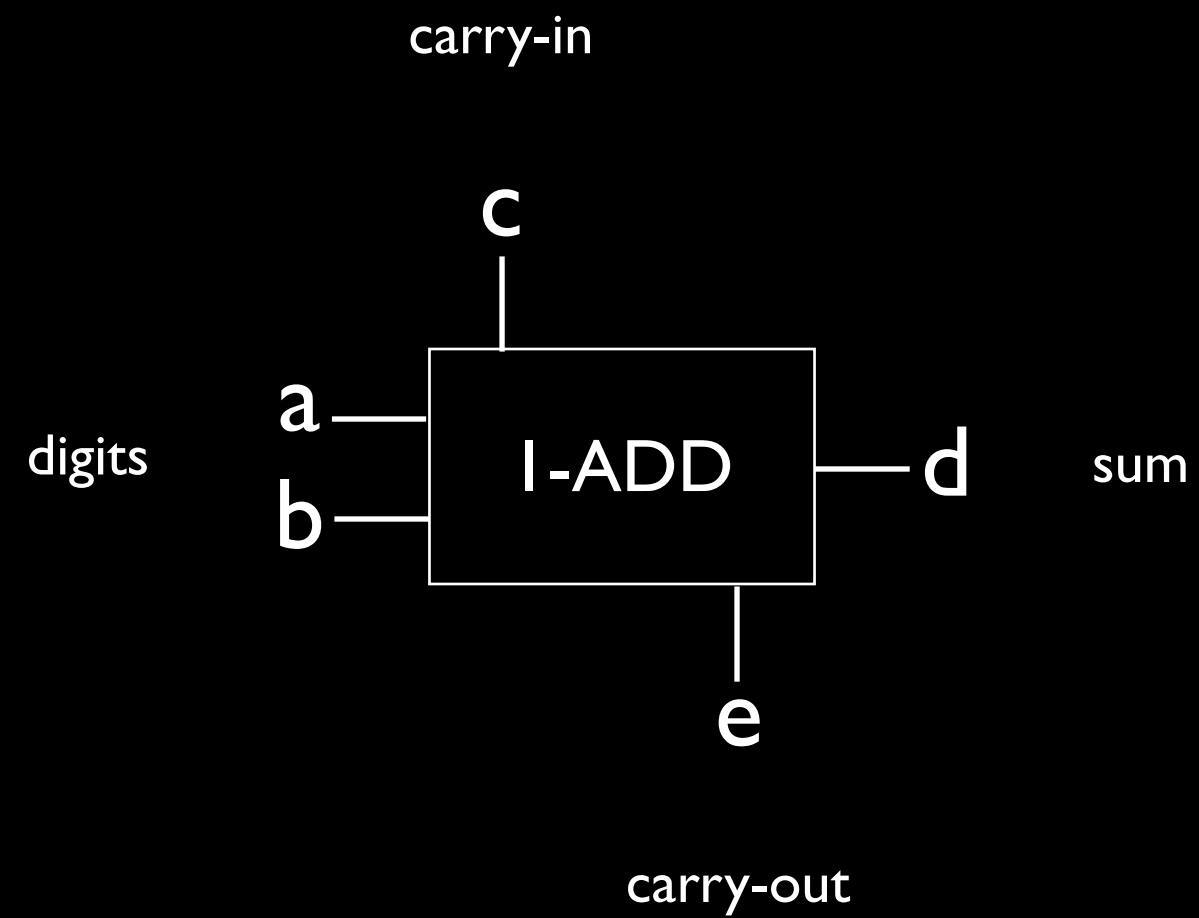


4-Bit Adder

 


4-Bit Adder

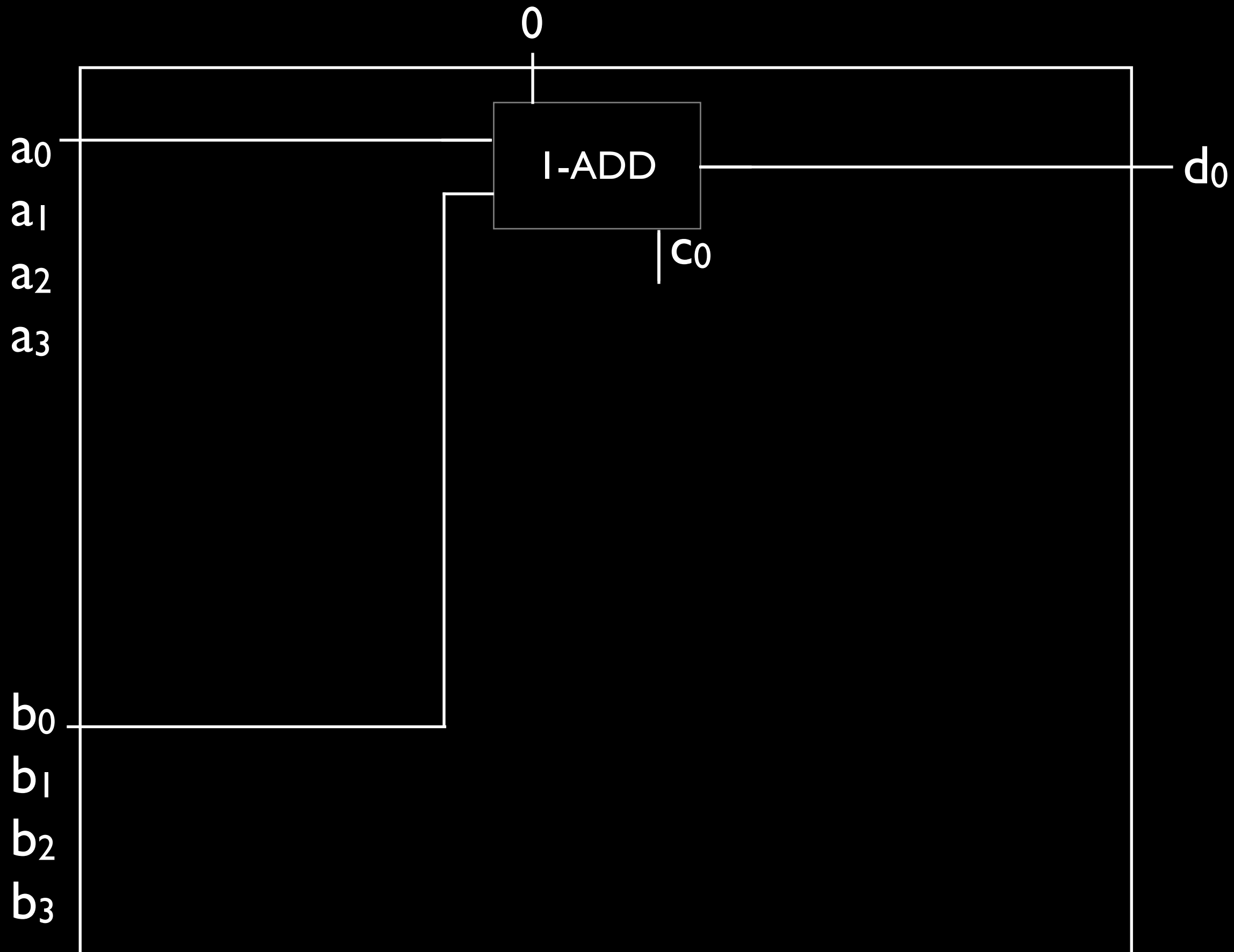


4-Bit Adder

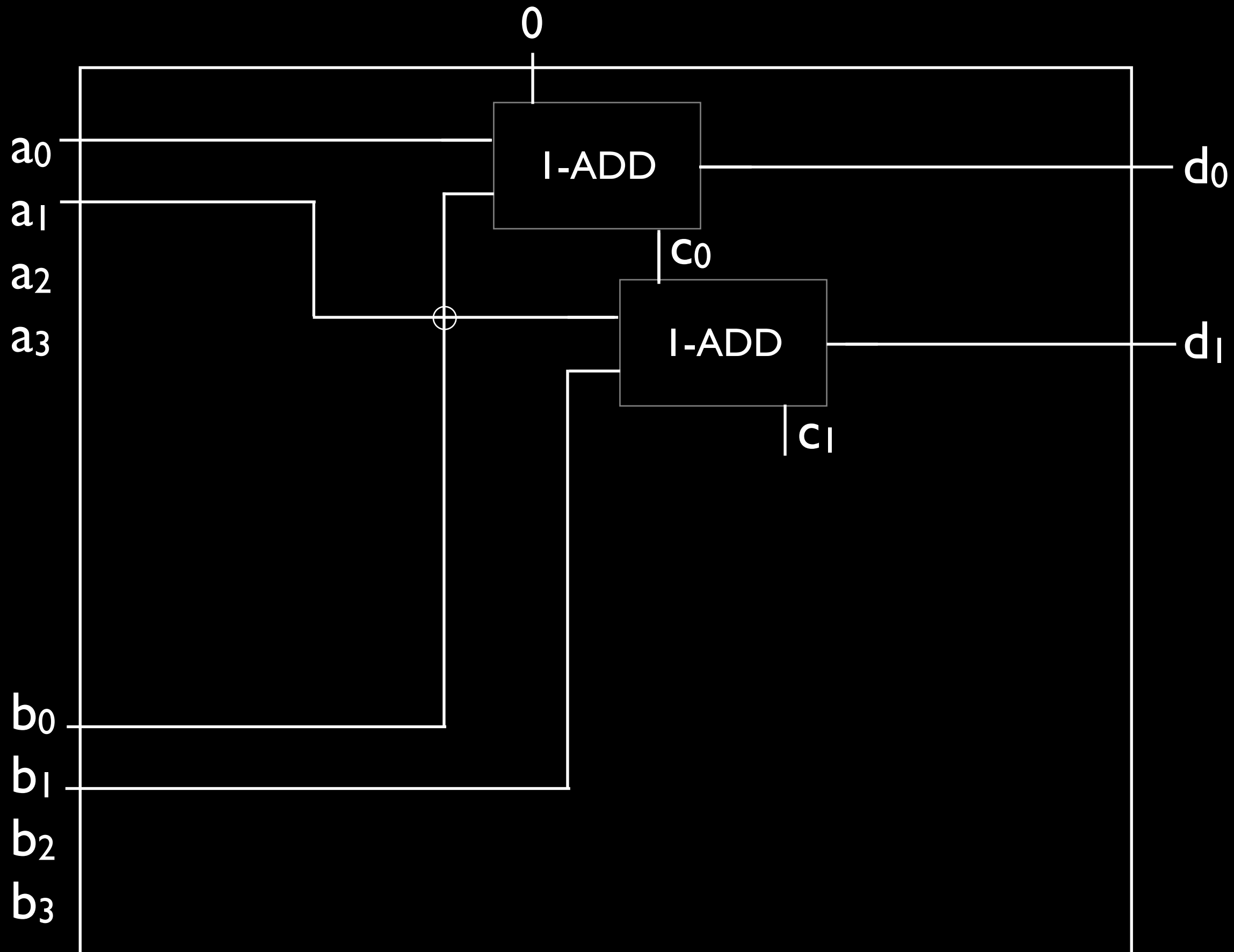

4-Bit Adder

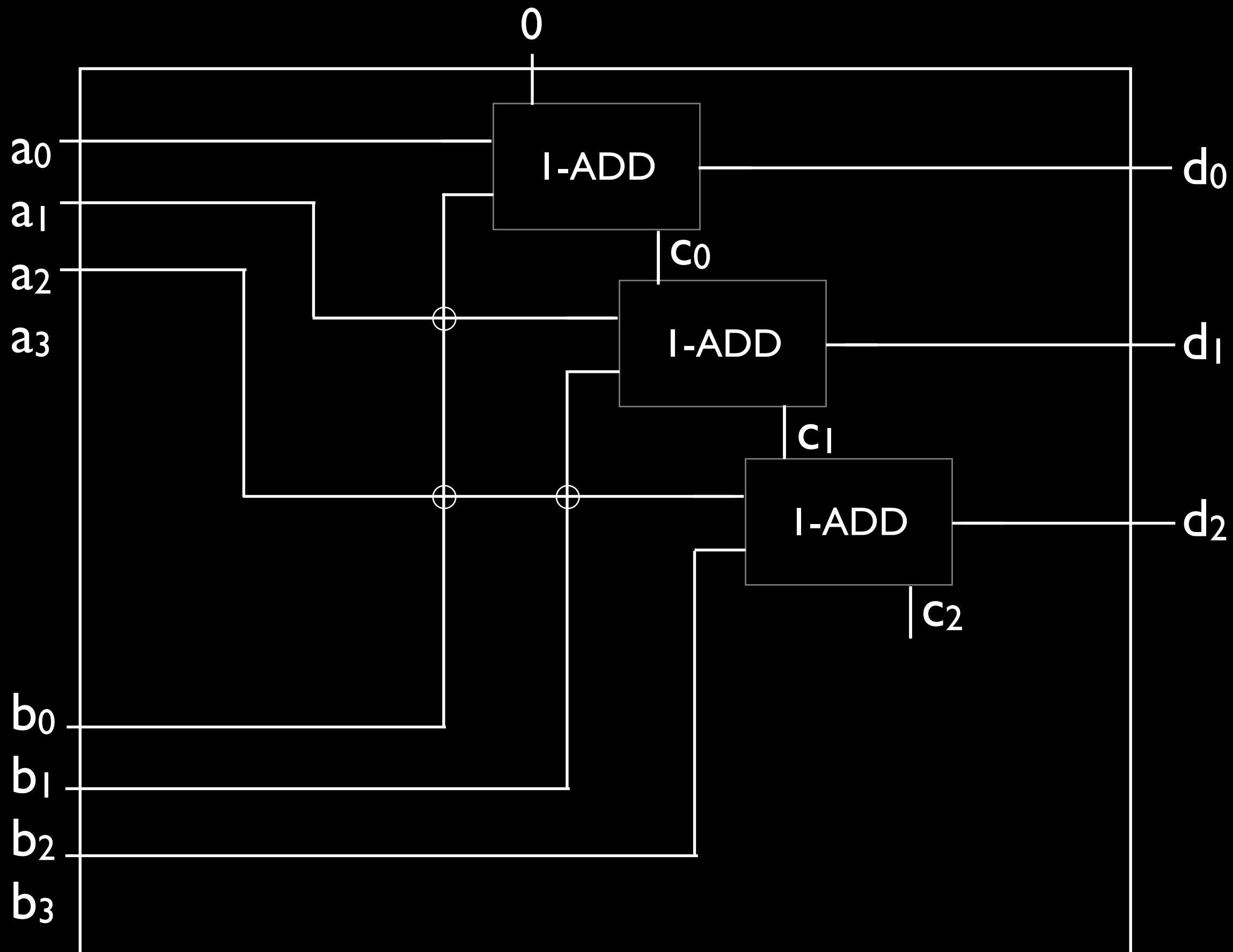

4-Bit Adder

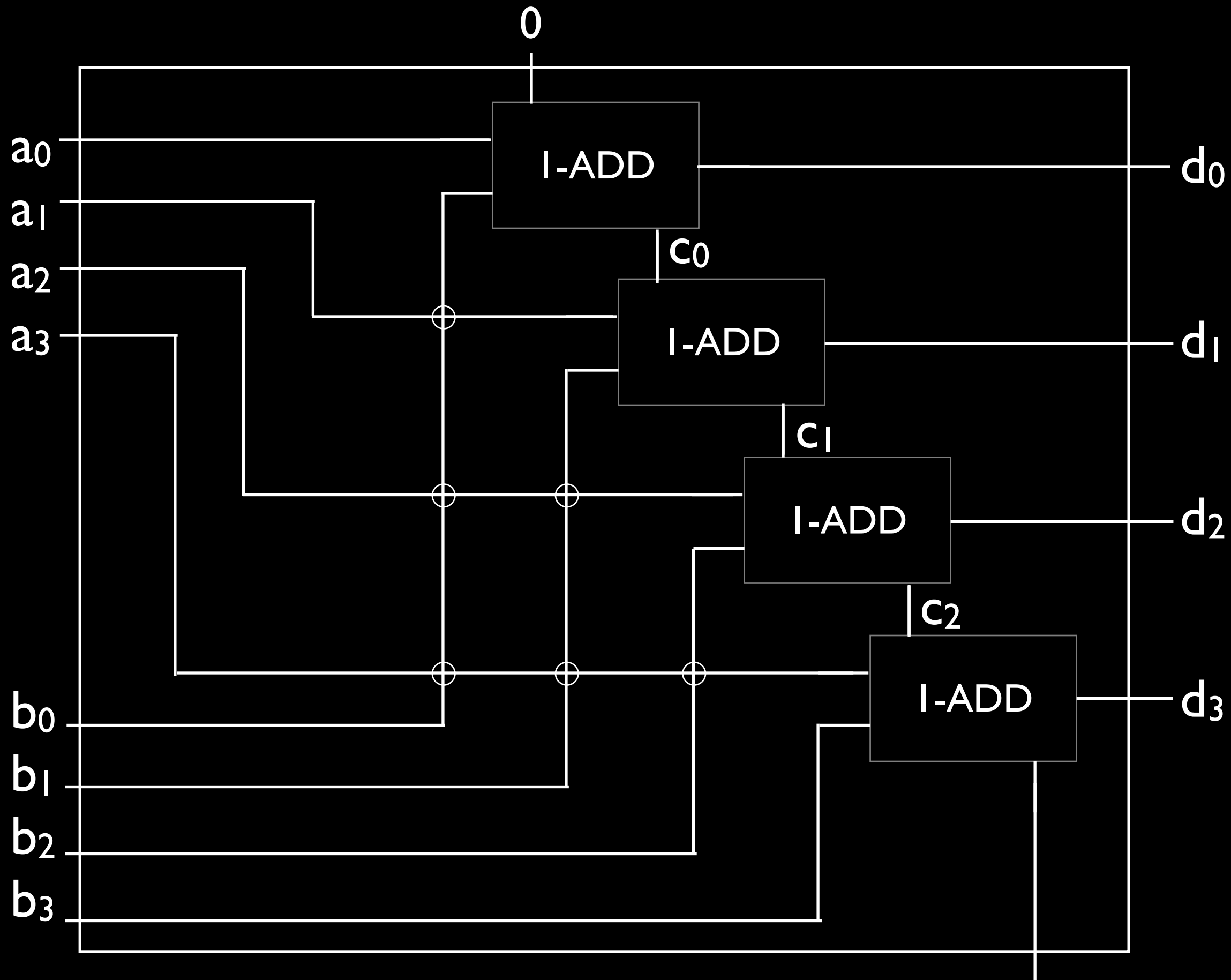


32-bit Adder

$96 = 32 \times 3$ *not* gates

$512 = 32 \times 16$ *and* gates

$192 = 32 \times 6$ *or* gates

800 gates

 

32-bit Adder


$96 = 32 \times 3$ *not* gates

$512 = 32 \times 16$ *and* gates

$192 = 32 \times 6$ *or* gates

800 gates

$1,504 = 96 + 1024 + 384$ transistors

 

32-bit Adder

$96 = 32 \times 3$ *not* gates

$512 = 32 \times 16$ *and* gates


$192 = 32 \times 6$ *or* gates

800 gates

$1,504 = 96 + 1024 + 384$ transistors

1945: refrigerator-sized computer

2015: .-sized computer

 

Equals 0

build a circuit that determines if an 8-bit number is 0

Equals 0

$$a_7 \ a_6 \ a_5 \ a_4 \ a_3 \ a_2 \ a_1 \ a_0 = 00000000$$

Equals 0

								output
a	b	c	d	e	f	g	h	i
⋮								⋮

How many rows?

Equals 0


a	b	c	d	e	f	g	h	i
0	0	0	0	0	0	0	0	1

Only one row has an output of 1


Equals 0

a	b	c	d	e	f	g	h	i
0	0	0	0	0	0	0	0	1


$$i = a' \cdot b' \cdot c' \cdot d' \cdot e' \cdot f' \cdot g' \cdot h'$$

 

Equals 0

 

Equals 0

 

Equals 0

